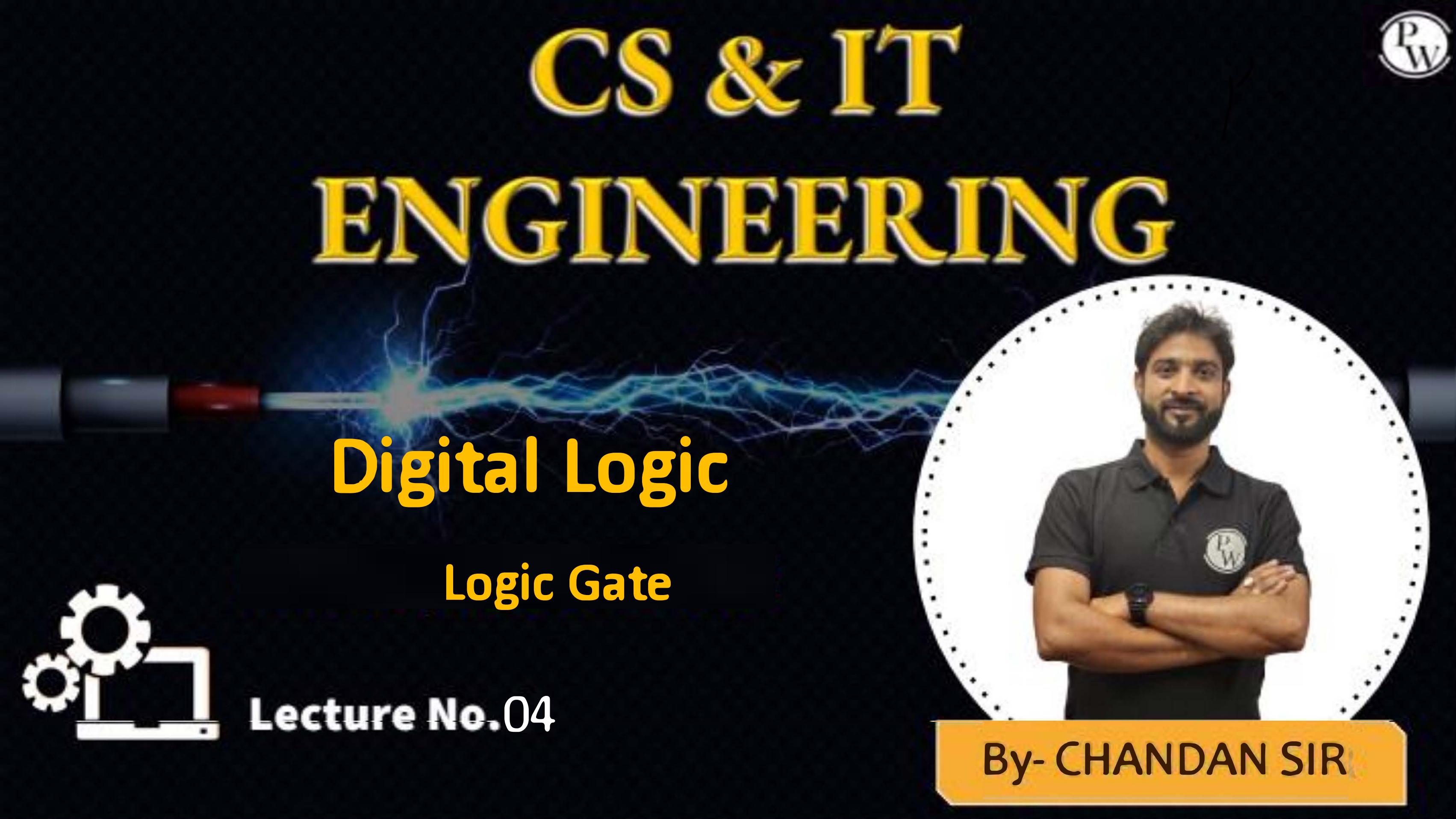


# CS & IT ENGINEERING



## Digital Logic

### Logic Gate



#### Lecture No. 04



By- CHANDAN SIR

## TOPICS TO BE COVERED


01 NAND GATE

02 NOR GATE




03 Discussion

INVERTER

-○-

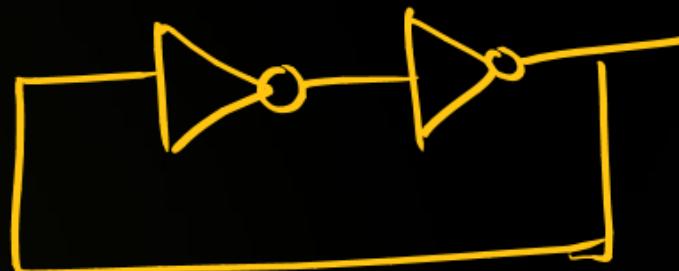

$$f = \frac{1}{2N \times C_{pd}}$$

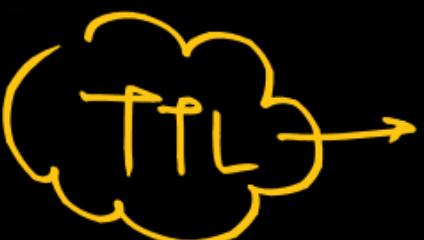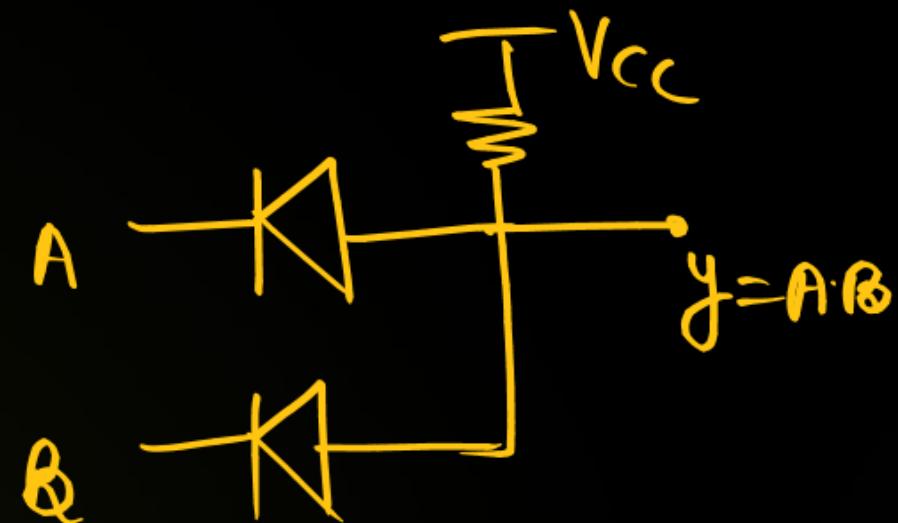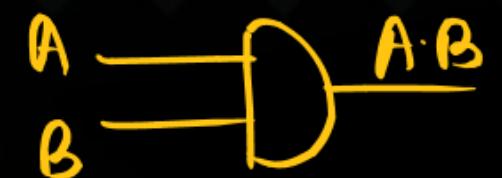
AND GATE

TTL




ECL

OR GATE

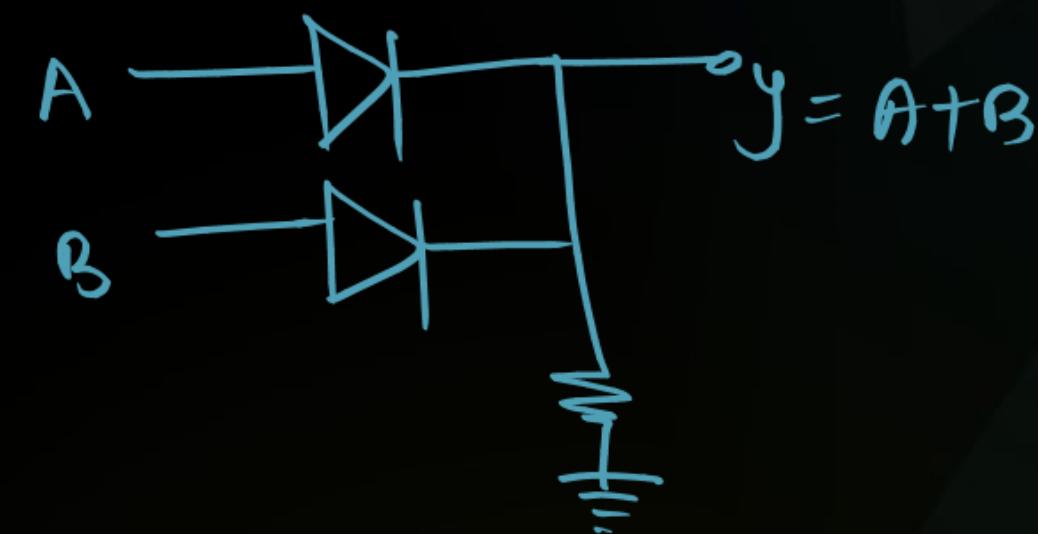

A	B	$A+B$
0	0	0
0	1	1
1	0	1
1	1	1

NAND

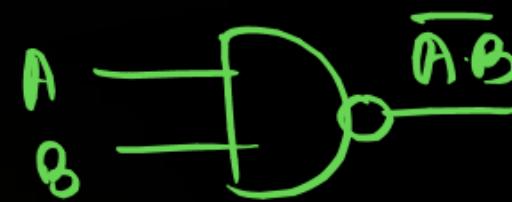


$$\bar{A} \cdot \bar{B} = \bar{B} \cdot \bar{A}$$

$$\overline{(\bar{A} \cdot \bar{B}) \cdot C} \neq \overline{\bar{A} \cdot (\bar{B} \cdot C)}$$



$\times \rightarrow$  Associative Law  $\times$

A	B	$Y = \bar{A} \cdot \bar{B}$
0	0	1
0	1	1
1	0	1
1	1	0

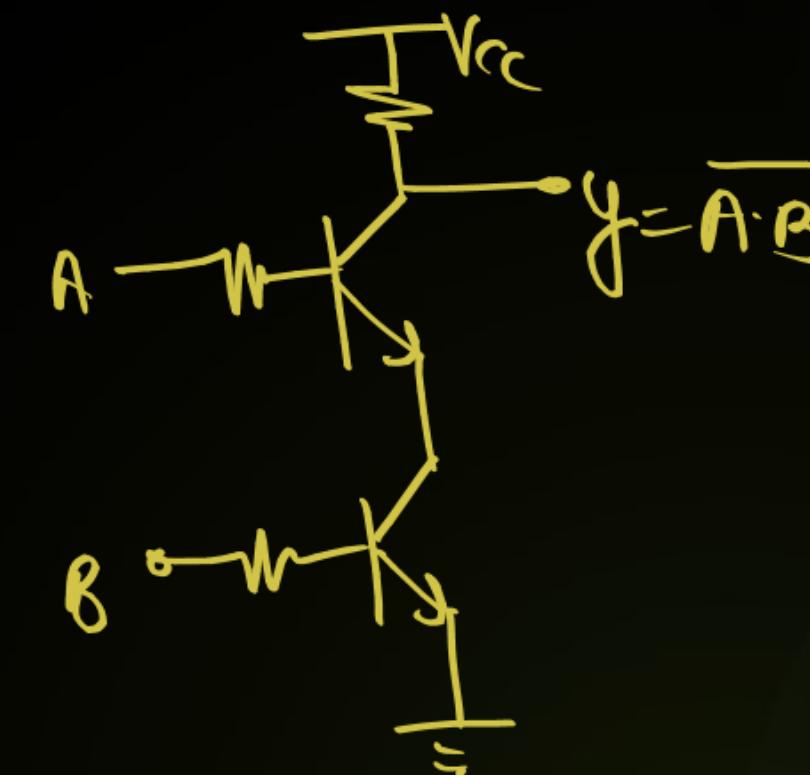


NOR GATE

$$\begin{array}{ccc} A & B & \overline{A+B} \end{array}$$

0	0	1
0	1	0
1	0	0
1	1	0

$$\overline{A+B} = \overline{B+A} \quad \text{commutative Law} \checkmark$$
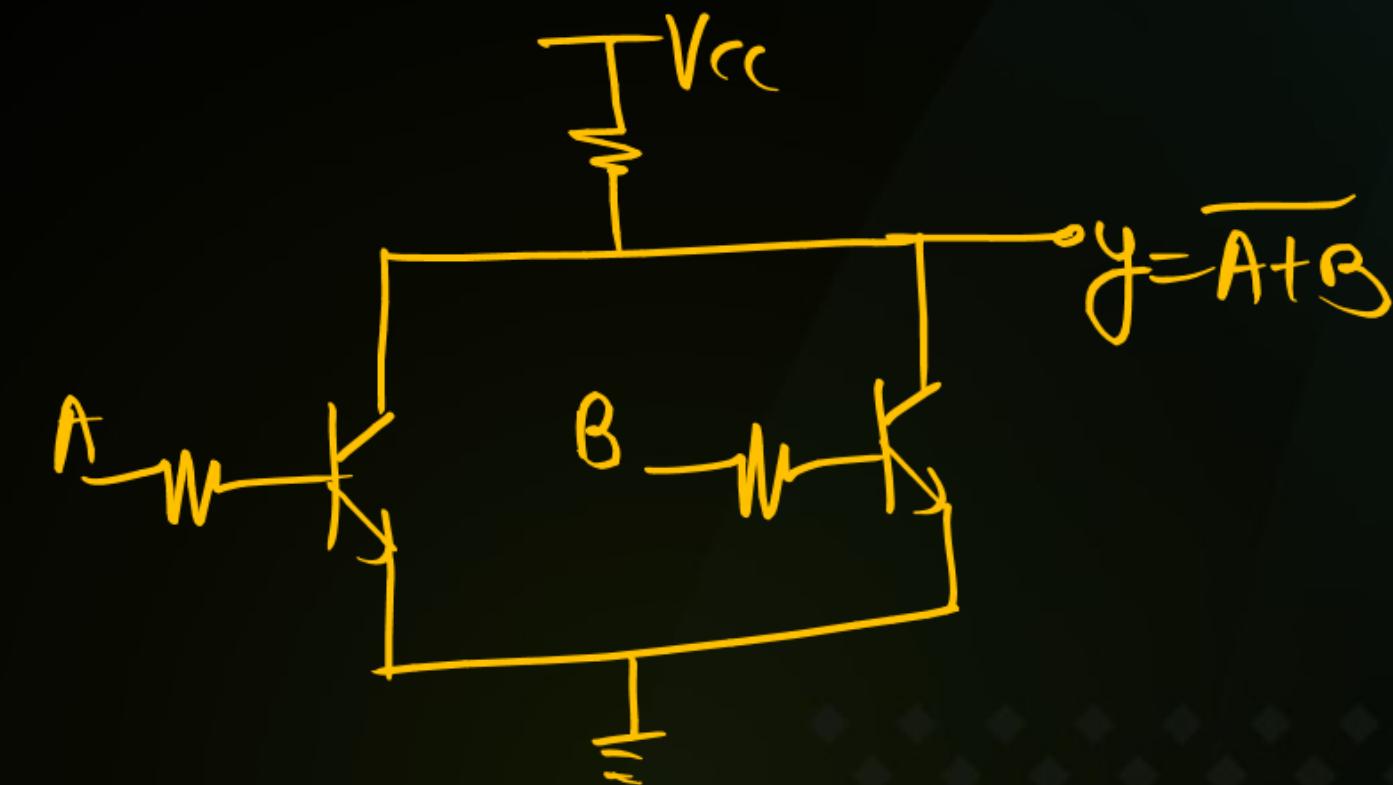
$$\overline{(A+B)+C} \neq \overline{A+(B+C)} \times$$



Q.

MSQ

P  
W

Which of the following option(s) is/are called universal logic?

- A  $(\overline{A} + B)$
- B  $(\overline{A} \cdot \overline{B})$
- C  $(A + \overline{B})$  ✓
- D  $A \cdot \overline{B}$


universal logic

$$\left. \begin{array}{l} \# \quad \overline{A \cdot B} \\ \# \quad \overline{A + B} \end{array} \right\}$$




Universal Logic

$$A + \bar{B}$$


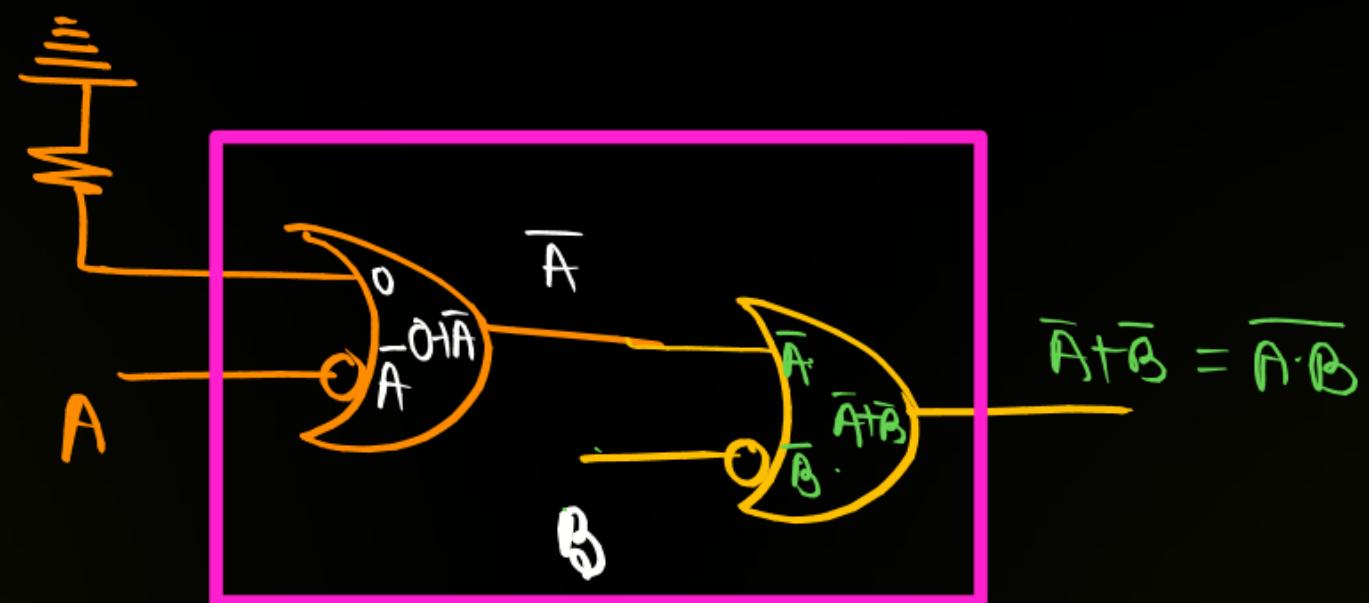


NAND

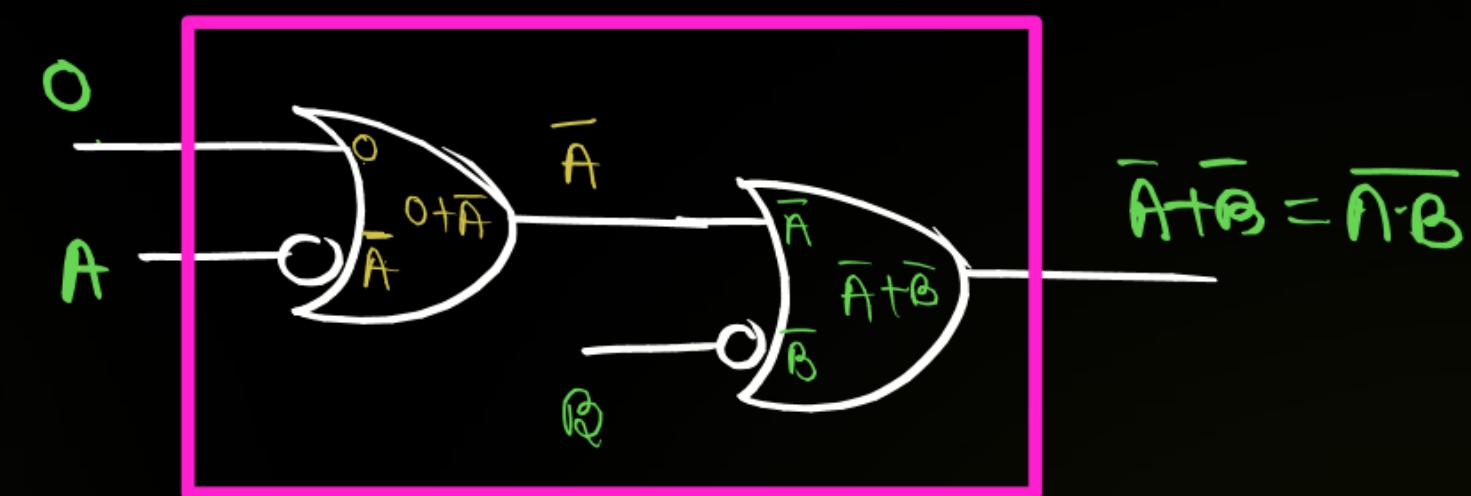

NAND

$$A \cdot \bar{B}$$

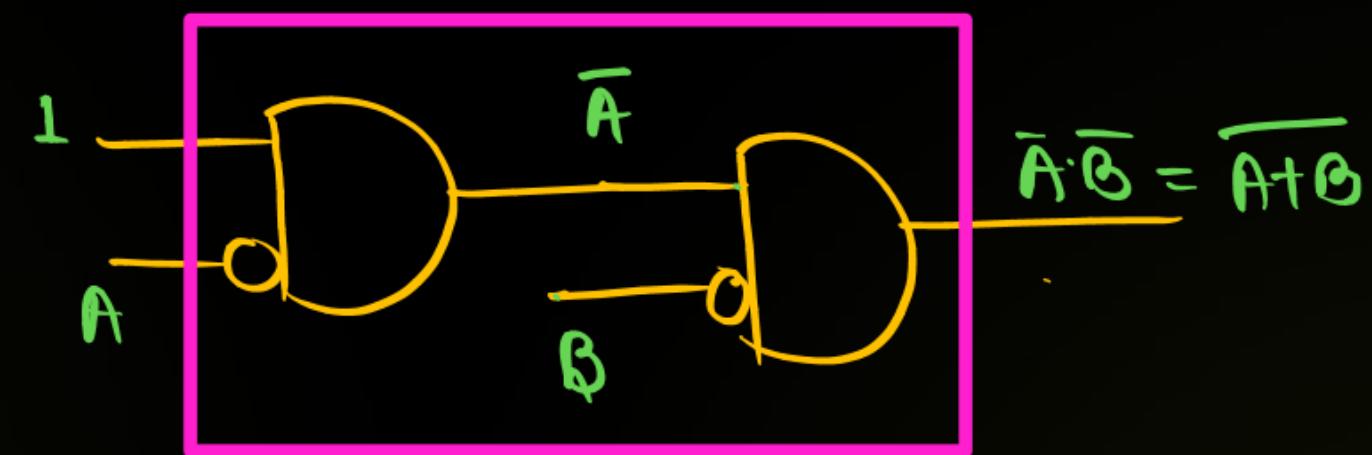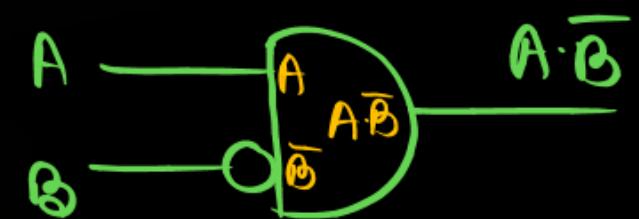

NOR

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

$$\overline{A} + B$$

$$A + \overline{B}$$


$$\overline{A} \cdot B$$

$$A \cdot \overline{B}$$

Multiplexer

Decoder + OR Logic

$\Rightarrow$  universal logic
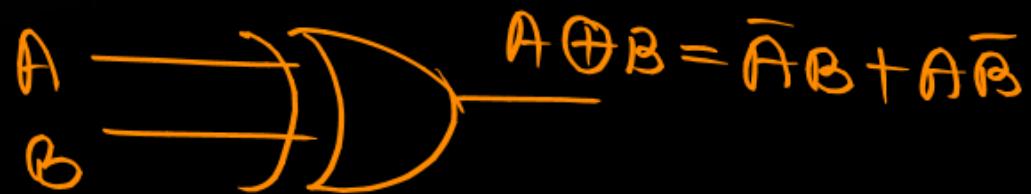
# X-OR GATE# X-NOR GATEDistribution Theorem

$$A+B+C = (A+B)(A+C)$$

Ex.

$$\begin{aligned} A+\bar{A}B &= (A+\bar{A})(A+B) \\ &= 1 \cdot (A+B) \\ &= A+B \end{aligned}$$

# NAND, NOR GATE

## NAND AS UNIVERSAL LOGIC


### 1. NOT GATE




### 2. AND GATE




### 3. OR GATE

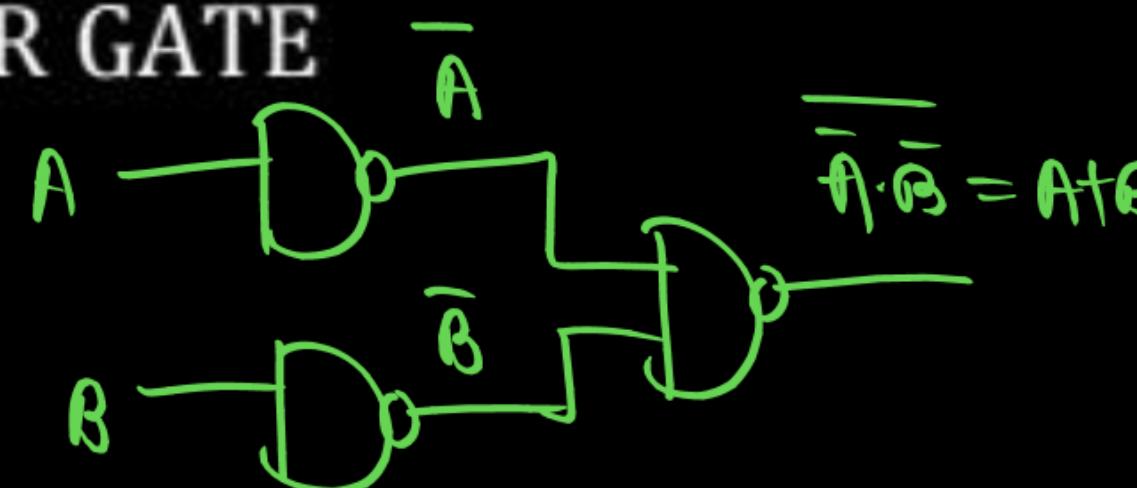


### 4. XOR GATE

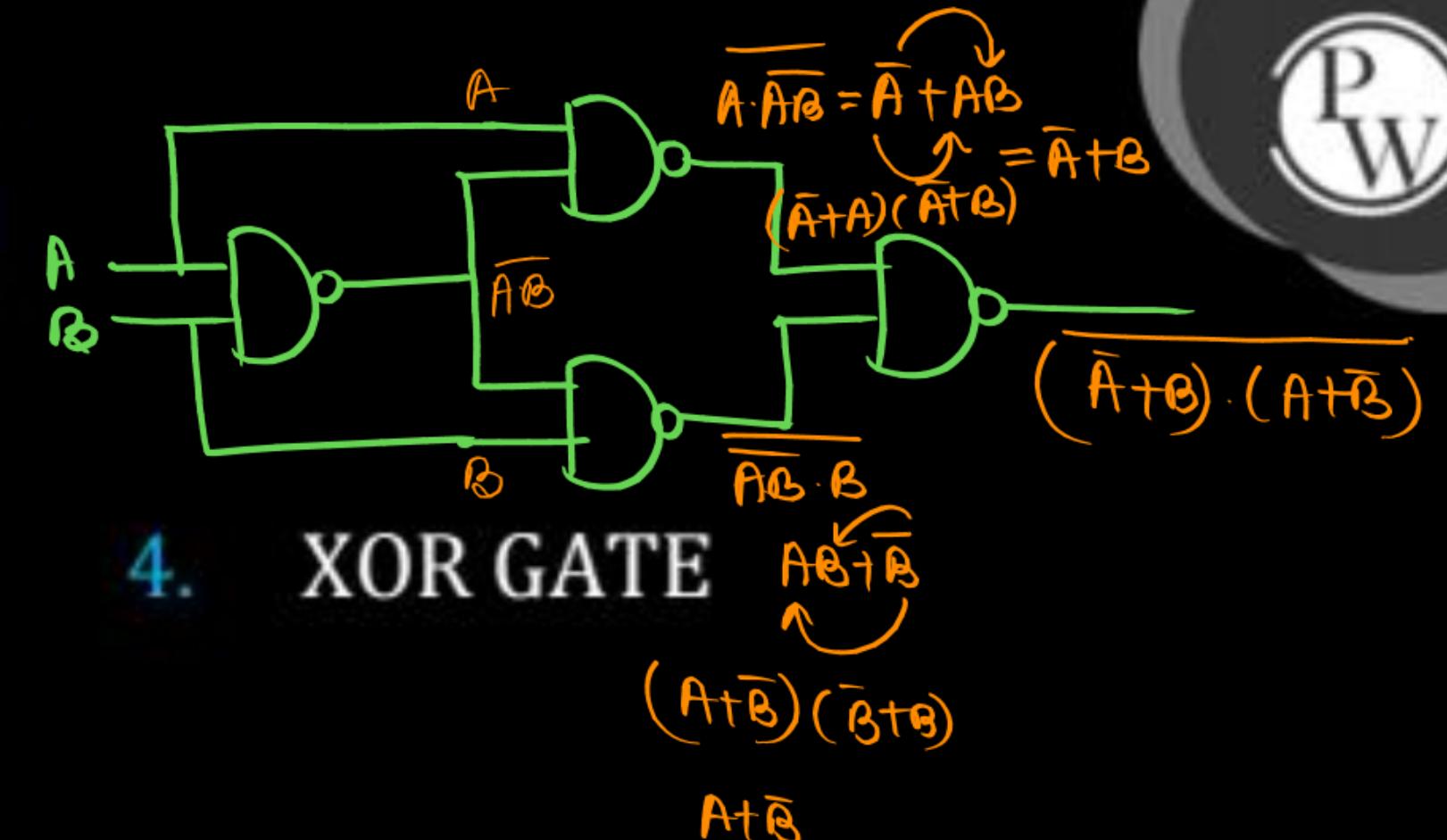

### 5. XNOR GATE

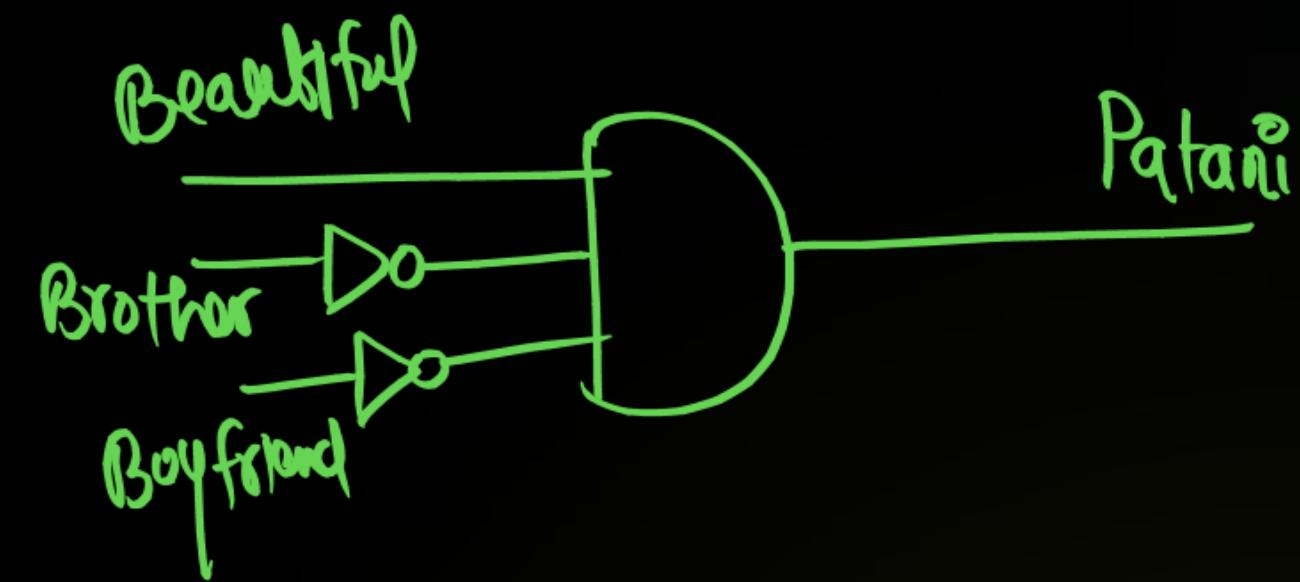


X-OR

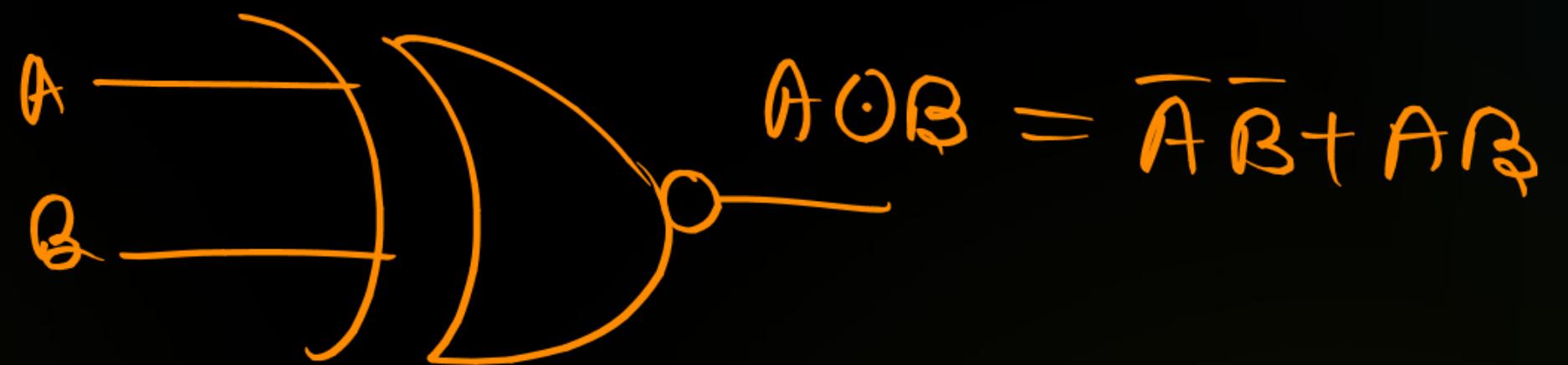X-NORlawTheorem


# Distribution theorem

$$A + B \cdot C = (A + B) (A + C)$$

$$x + yz = (x+y)(x+z)$$

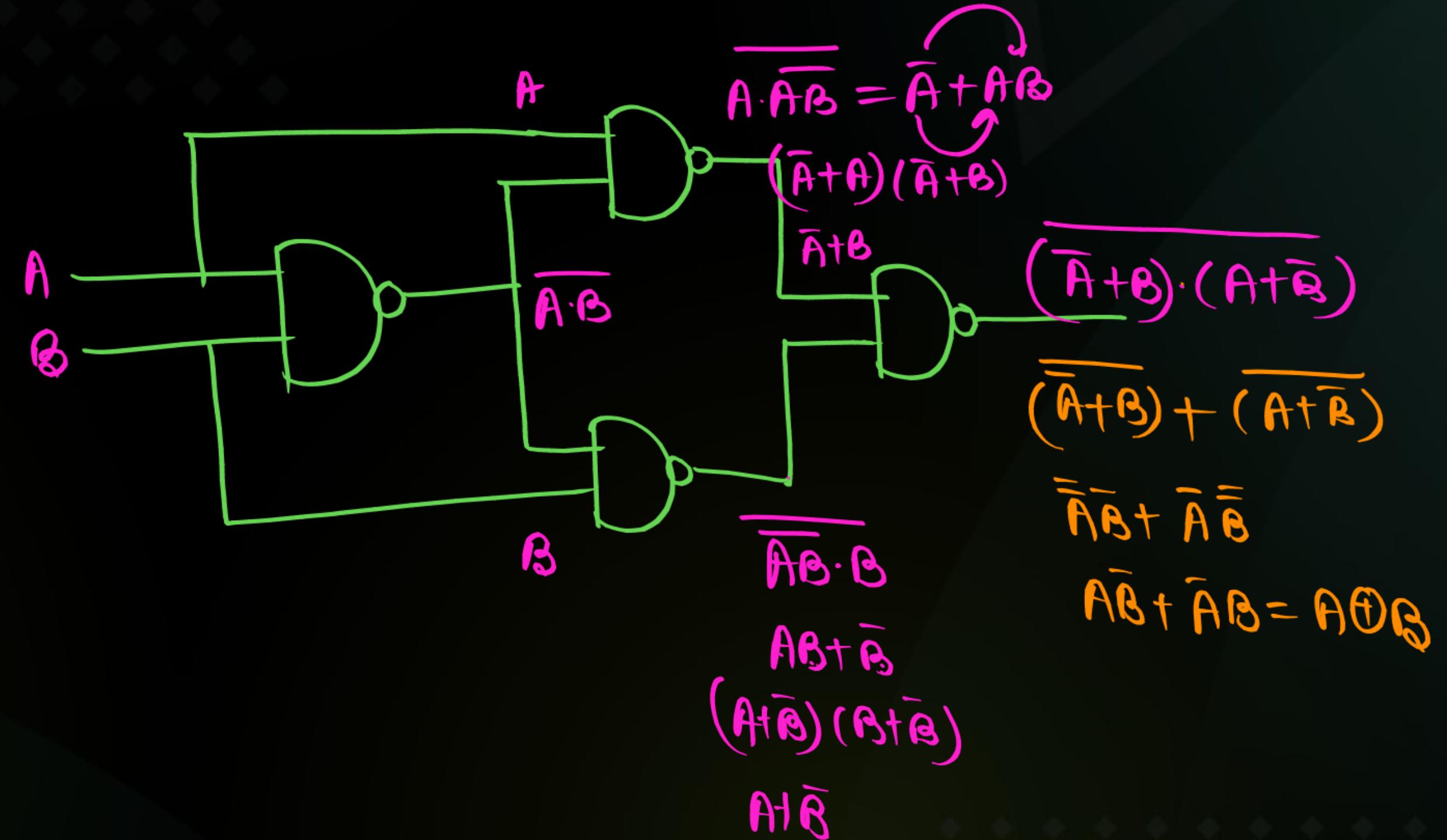

Telegram  $\rightarrow$  t.me/cjsir

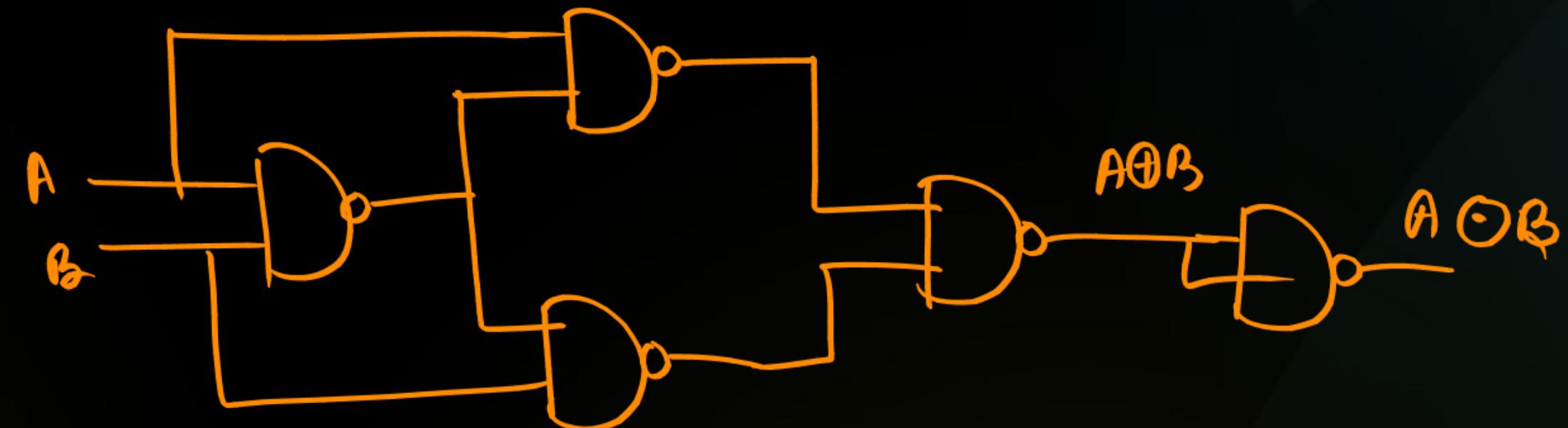


	NAND	NOR
NOT	1	1
AND	2	3
OR	3	2
X-OR	4	5
X-NOR	5	4
NAND	1	4
NOR	4	1

Q Find the minimum no. of two input NAND GATE required to implement the logic given below—

$$f(A, B, C) = \bar{A} \cdot BC$$

- (A) 3
- (B) 4
- (C) 5
- (D) None

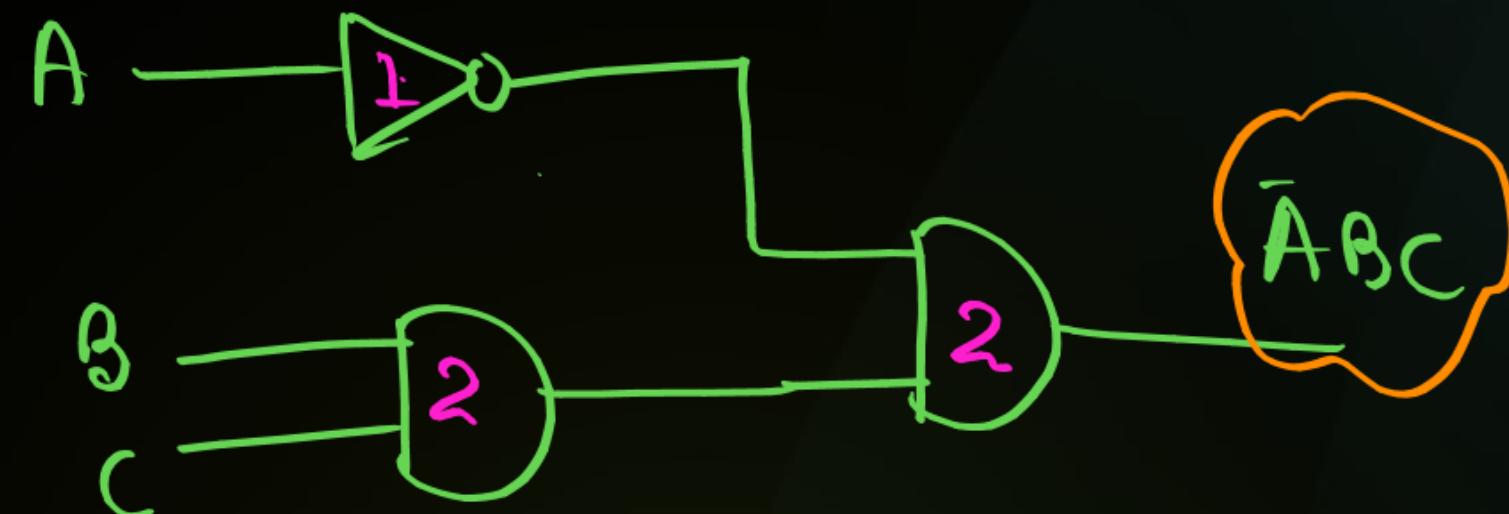



$$1 + 2 + 2 = 5$$

Q Find the minimum no. of two input NAND GATE required to implement the logic given below?

$$f(A, B, C, D) = AB + CD$$

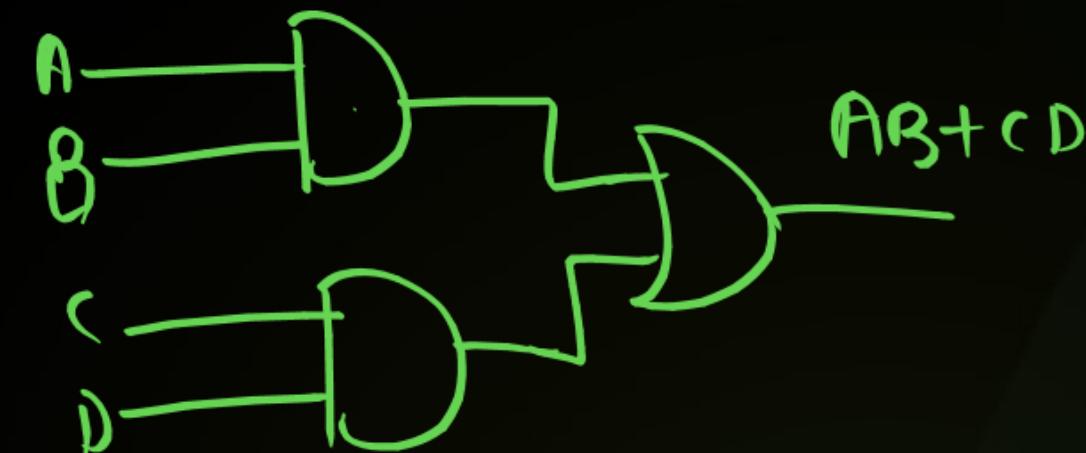- (A) 1  
~~(B) 3~~  
~~(C) 7~~  
~~(D) 5~~



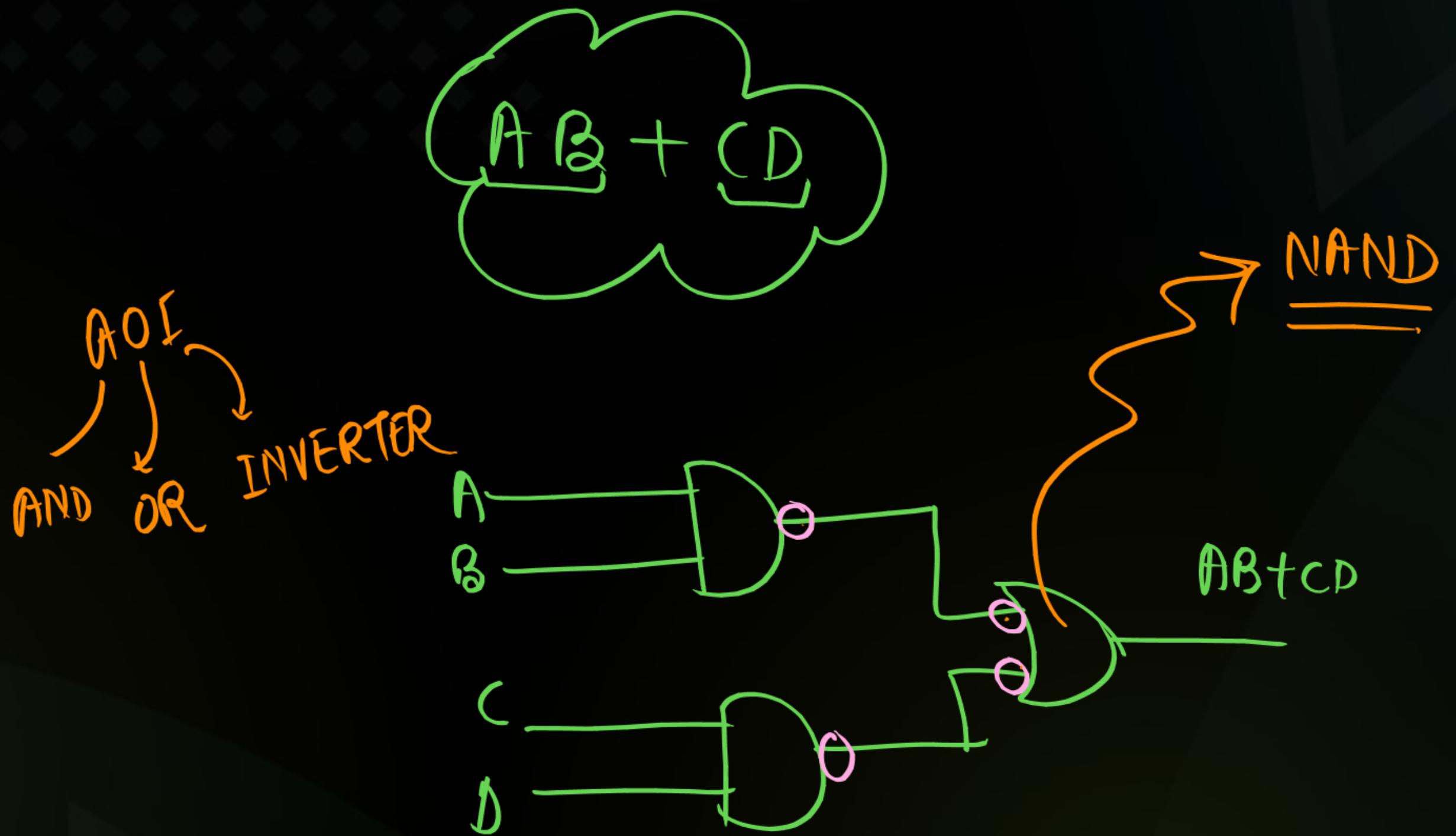


$\emptyset$  $\underline{\underline{A + BC}}$  $NAND = 2$  $=$

**Q.**

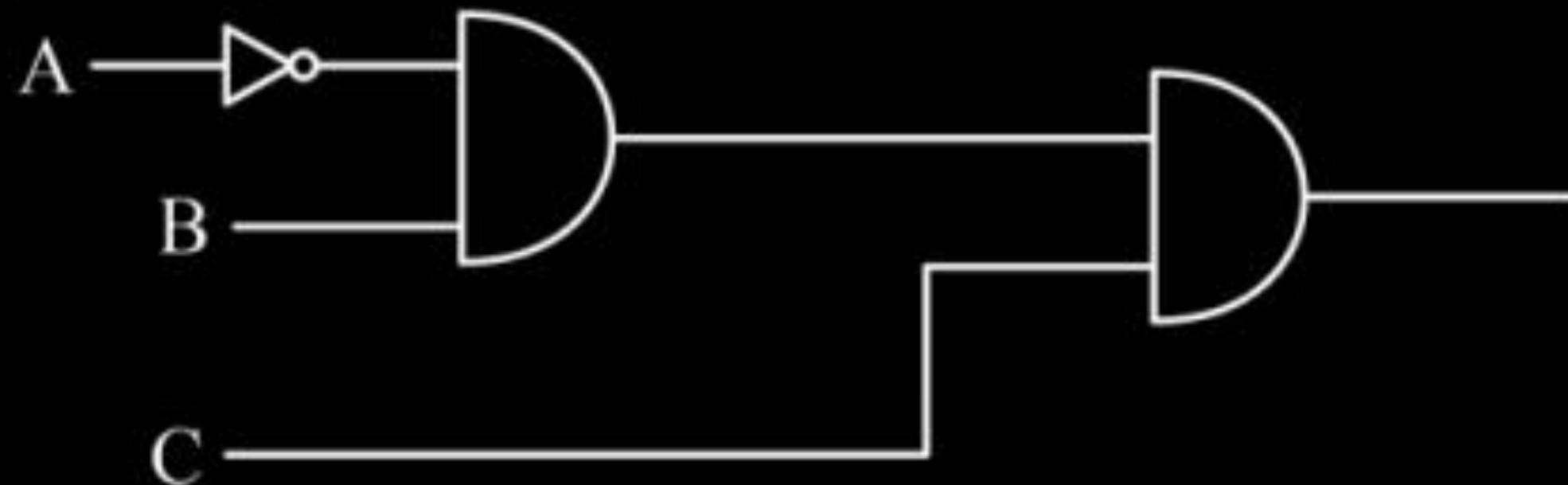**NAT**



P  
W

For the following circuit diagram minimum numbers two NAND gate required.



## NAND, NOR GATE

- Alternate Symbol

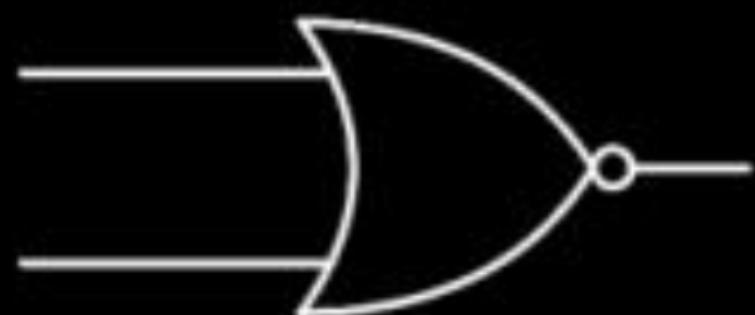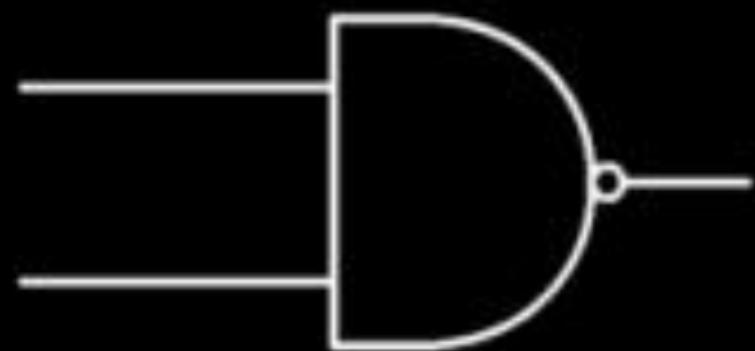

Telegram channel

Thank you

et me/cj sir

**GW**  
*Soldiers !*

